

**MAT 399****Quiz 2****Fall 2025**

1. Consider the quantum circuit which applies a Hadamard gate to the first qubit followed by a standard CNOT gate with first qubit control and second qubit target such that the second qubit is flipped only when the first qubit equals 1. If  $A$  is the  $4 \times 4$  matrix of this circuit (with respect to the computational basis), which of the following is a scalar multiple of the third column?

a)  $\begin{pmatrix} 1 \\ 0 \\ 1 \\ 0 \end{pmatrix}$       b)  $\begin{pmatrix} 0 \\ 1 \\ 0 \\ 1 \end{pmatrix}$       c)  $\begin{pmatrix} -1 \\ 1 \\ -1 \\ 1 \end{pmatrix}$       d)  $\begin{pmatrix} -1 \\ 0 \\ -1 \\ 0 \end{pmatrix}$       e)  $\begin{pmatrix} 1 \\ 0 \\ 0 \\ -1 \end{pmatrix}$

Correct Answer:  $\begin{pmatrix} 1 \\ 0 \\ 0 \\ -1 \end{pmatrix}$

2. Same circuit as in the previous problem. If both input qubits are set to  $|0\rangle$ , what is the output in the computational basis?

a)  $\frac{1}{\sqrt{2}}(|01\rangle + |10\rangle)$       b)  $\frac{1}{\sqrt{2}}(|00\rangle - |11\rangle)$       c)  $\frac{1}{\sqrt{2}}(|00\rangle + |11\rangle)$       d)  $\frac{1}{\sqrt{2}}(|01\rangle - |11\rangle)$   
e)  $\frac{1}{\sqrt{2}}(|00\rangle - |11\rangle)$

Correct Answer:  $\frac{1}{\sqrt{2}}(|00\rangle + |11\rangle)$

3. Same circuit as in the previous problem. If both input qubits are set to  $|0\rangle$ , and the final output is measured on both wires in the computational basis, what is the probability that the measurement will yield the basis state  $|00\rangle$ ?

a)  $\frac{1}{2}$       b)  $\frac{1}{\sqrt{2}}$       c)  $\frac{1}{4}$       d) 0      e) 1

Correct Answer:  $\frac{1}{2}$

4. Same circuit as in the previous problem. If both input qubits are set to  $|0\rangle$ , and the final output is measured on both wires in the computational basis, what is the probability that the measurement will yield the basis state  $|10\rangle$ ?

a)  $\frac{1}{2}$       b)  $\frac{1}{\sqrt{2}}$       c)  $\frac{1}{4}$       d) 0      e) 1

Correct Answer: 0

5. Let  $f : \{0, 1\}^2 \rightarrow \{0, 1\}$  be a Deutsch-Jozsa oracle function which is obtained from a standard CNOT circuit acting on the computational basis of  $\mathbb{H}_2 = \mathbb{H}_1 \otimes \mathbb{H}_1$  by using input string  $ab$  converted to input  $|a\rangle|b\rangle$  and using the output on the second qubit wire  $|y\rangle$  so that  $f(ab) = y$ . True or False:

i)  $f$  is balanced      ii)  $f(00) = 1$       iii)  $f(11) = 0$   
a) TTT      b) FTT      c) TTF      d) TFF      e) TFT

Correct Answer: TFT

6. Let  $f : \{0,1\}^2 \longrightarrow \{0,1\}$  be a Deutsch-Jozsa oracle function (so  $f$  is assumed to be either constant or balanced) with the property that  $f(00) = 1$  and  $f(11) = 0$ . Also suppose a quantum circuit implements  $f$  with three wires (as done in class). So the first two wires will accept a bit string  $s$  of length two converted to two kets (left to right becomes top to bottom on the wires) and last (bottom wire) is always given input  $|0\rangle$ . The last wire produces the output ket  $|y\rangle$  so that the function takes value  $f(s) = y$ . Also, suppose that the circuit consists of blocks with combinations of  $X$  and CCNOT gates (as done in class) and contains the following block: a single  $X$  on the first wire, followed by a CCNOT, followed by an  $X$  again on the first wire. This information implies which of the following?

- |                    |                 |                  |
|--------------------|-----------------|------------------|
| i) $f$ is balanced | ii) $f(01) = 1$ | iii) $f(10) = 0$ |
| a) TTT             | b) FTT          | c) TTF           |
|                    |                 | d) TFF           |
|                    |                 | e) TFT           |

Correct Answer: TTT